
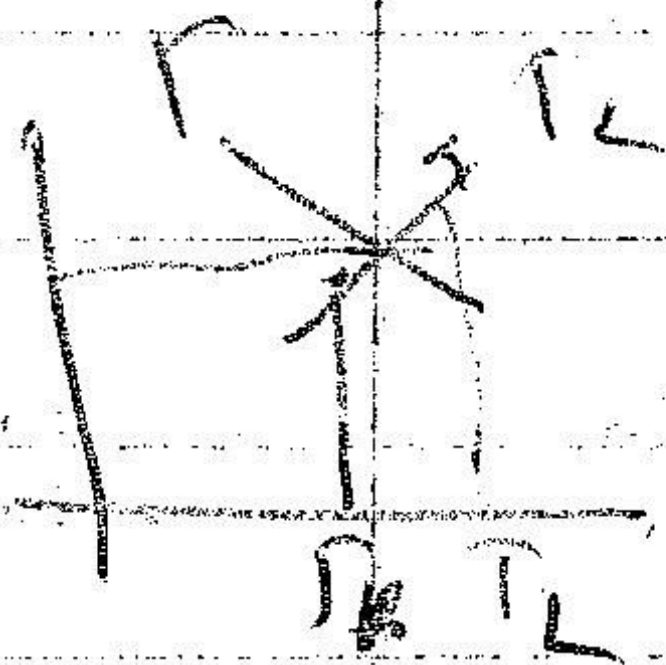
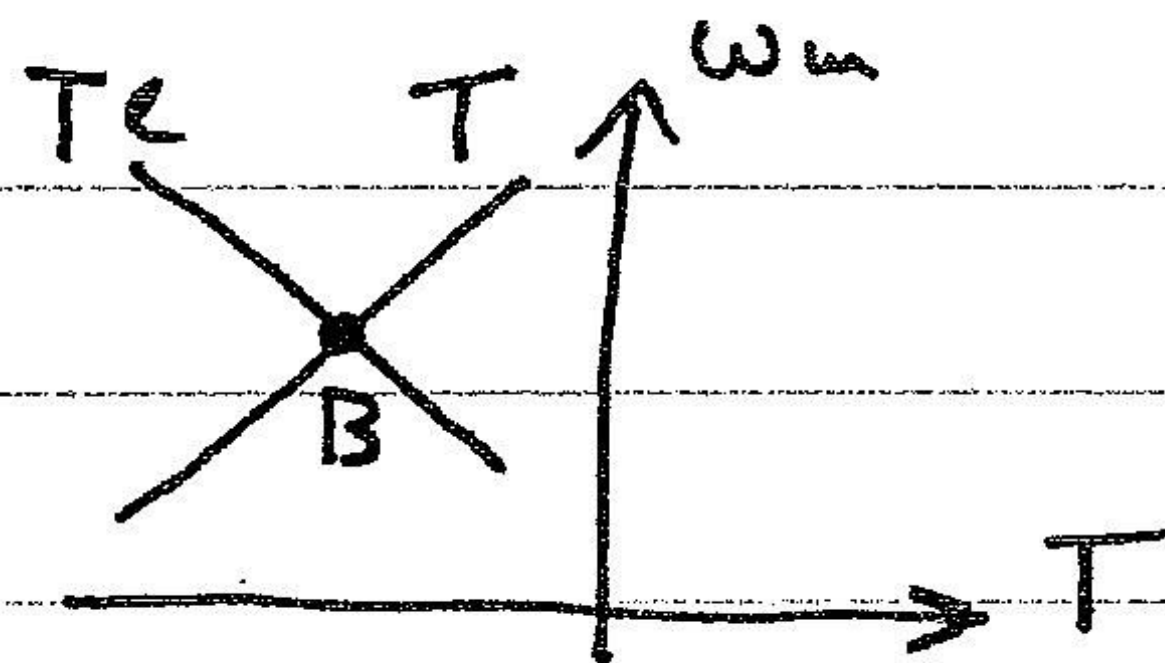


DC drives 1^o EXAM

- Q1) What is meant by electrical drives? Draw the block diagram of an electrical drive.
- b. Draw the block diagrams of the available AC to DC converters.
- c. What are the disadvantages of DC motors?
- d. What does the choice of an electrical drive depend on?

- Q2) Write the equation of the components of load torque.
- b. Draw the speed-torque characteristic of high speed hoist and traction load.

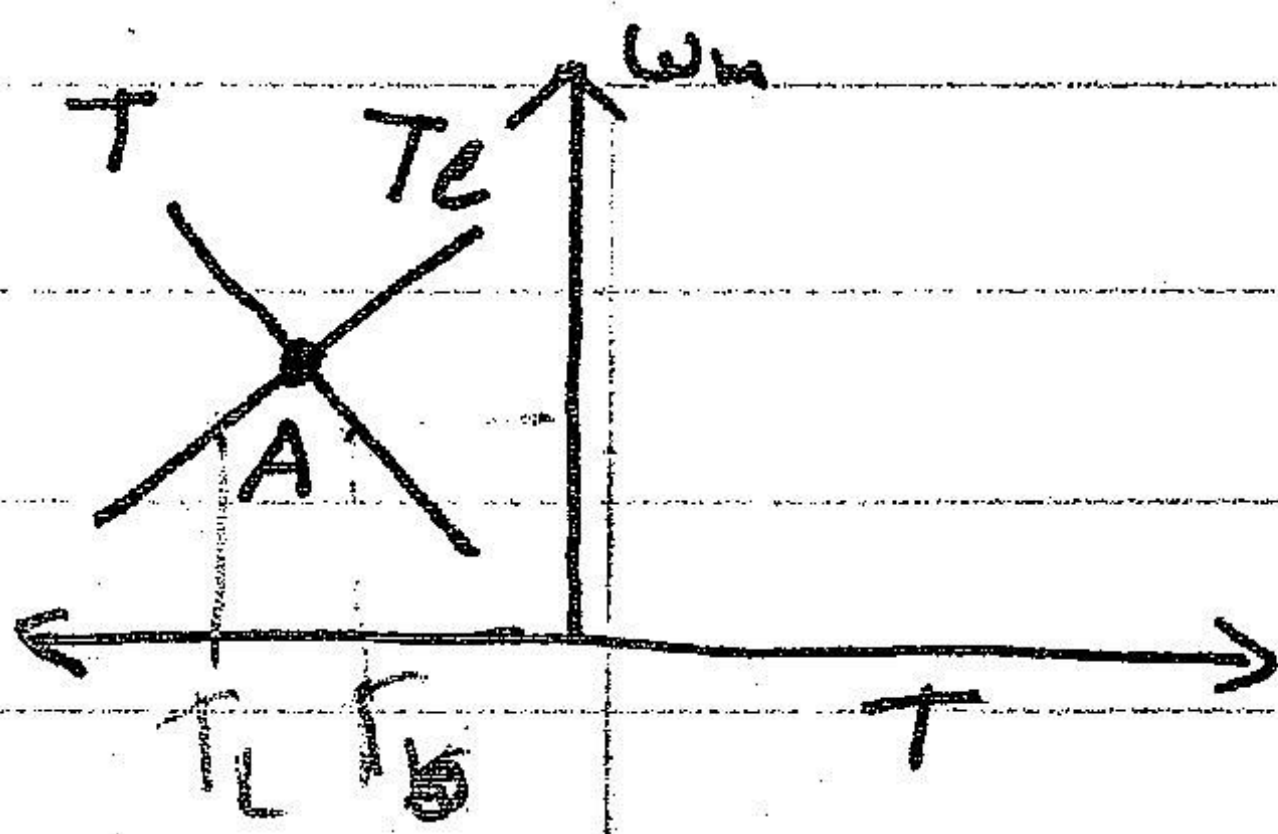- Q3) Find out if points A and B are stable or not. Why?




الامتحان الأول
DC Drives

تم الرفع بواسطة م. محمد أبو عيسى

Q4) for the following hoist

5.5 a) show the direction of ω_m , T_e and T .

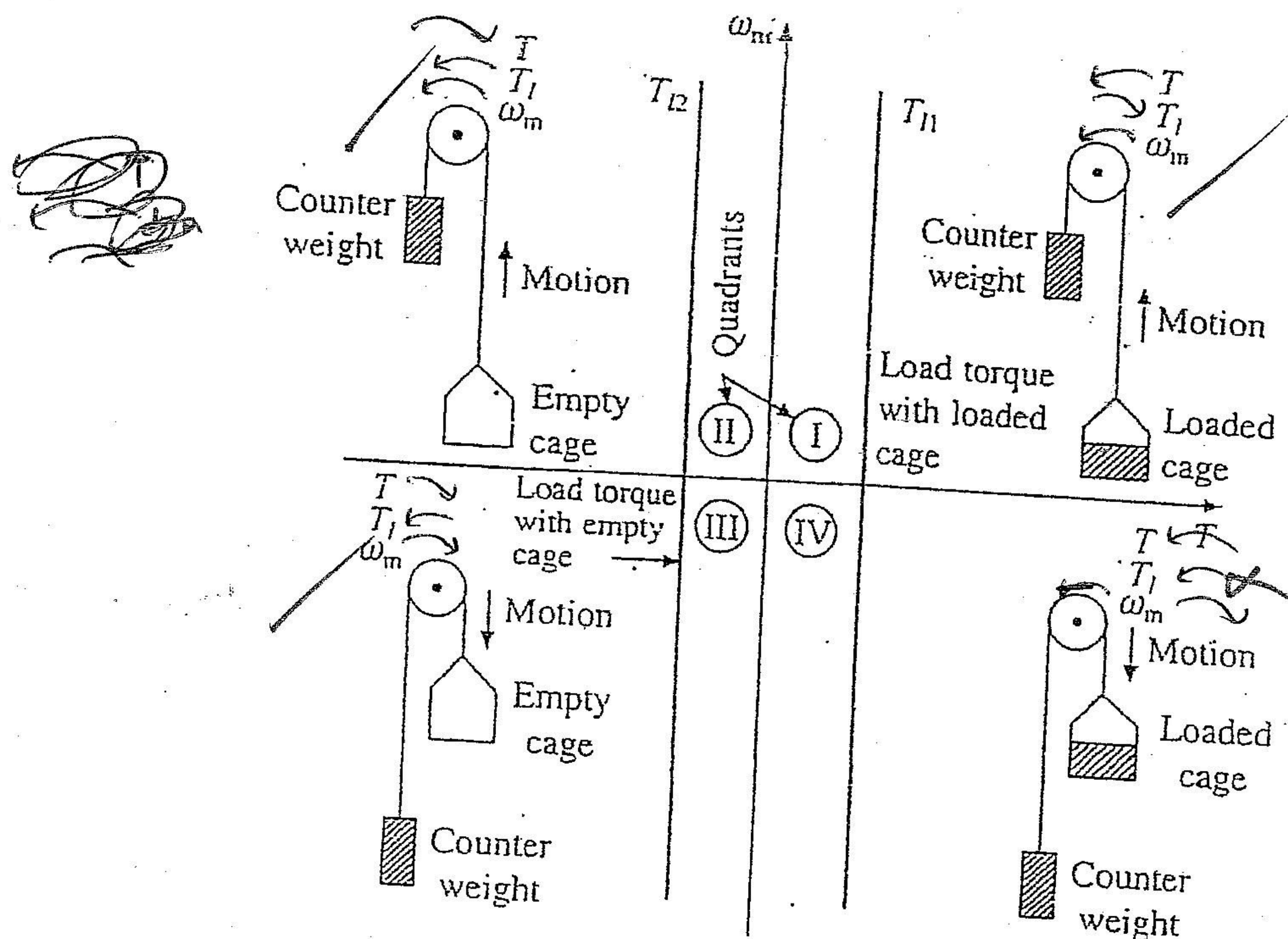
b) explain the operation of the motor in quadrant IV.



Q5) for the following system find

a. The total equivalent torque.

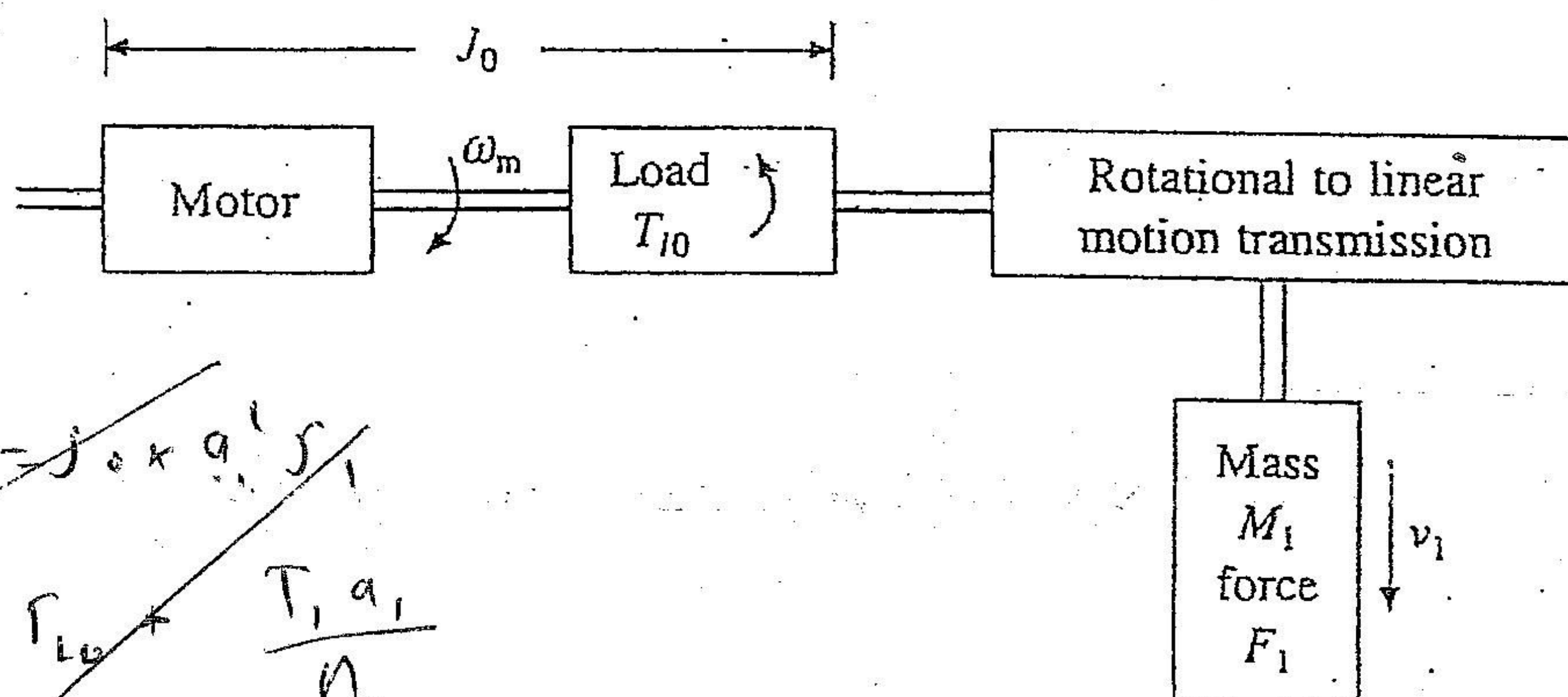b. The total equivalent moment of inertia.



~~$$J = J_0 + a_1^2 J_1$$~~

~~$$T = T_{L0} + \frac{T_1 a_1}{n_1}$$~~

~~$$J = J_0 + M \left(\frac{v}{\omega_m} \right)^2$$~~

~~$$T = T_{L0} + \frac{F}{n_1} \left(\frac{v}{\omega_m} \right)$$~~